

1

Sample Quiz 6  
Solutions

problem 1. Resistive Network with 2 Loops and DC Sources

(a) The system in augmented matrix form is

$$\left( \begin{array}{ccc|c} 1 & -1 & -1 & 0 \\ 4 & 2 & 0 & 28 \\ 0 & 2 & -1 & 7 \end{array} \right)$$

$$\left( \begin{array}{ccc|c} 1 & -1 & -1 & 0 \\ 0 & 6 & 4 & 28 \\ 0 & 2 & -1 & 7 \end{array} \right) \text{ combo}(1,2,-4)$$

$$\left( \begin{array}{ccc|c} 1 & -1 & -1 & 0 \\ 0 & 0 & 7 & 7 \\ 0 & 2 & -1 & 7 \end{array} \right) \text{ combo}(3,2,-3)$$

$$\left( \begin{array}{ccc|c} 1 & -1 & -1 & 0 \\ 0 & 2 & -1 & 7 \\ 0 & 0 & 7 & 7 \end{array} \right) \text{ swap}(2,3)$$

$$\left( \begin{array}{ccc|c} 1 & -1 & -1 & 0 \\ 0 & 2 & -1 & 7 \\ 0 & 0 & 1 & 1 \end{array} \right) \text{ mult}(3, 1/7)$$

$$\left( \begin{array}{ccc|c} 1 & -1 & -1 & 0 \\ 0 & 2 & 0 & 8 \\ 0 & 0 & 1 & 1 \end{array} \right) \text{ combo}(3,2,1)$$

$$\left( \begin{array}{ccc|c} 1 & -1 & 0 & 1 \\ 0 & 2 & 0 & 8 \\ 0 & 0 & 1 & 1 \end{array} \right) \text{ combo}(3,1,1)$$

$$\left( \begin{array}{ccc|c} 1 & -1 & 0 & 1 \\ 0 & 1 & 0 & 4 \\ 0 & 0 & 1 & 1 \end{array} \right) \text{ mult}(2, 1/2)$$

$$\left( \begin{array}{ccc|c} 1 & 0 & 0 & 5 \\ 0 & 1 & 0 & 4 \\ 0 & 0 & 1 & 1 \end{array} \right) \text{ combo}(2,1,1)$$

Last frame test passed ✓

## Sample Quiz 6, Solutions

Solution:  $\left\{ \begin{array}{l} I_1 = 5 \\ I_2 = 4 \\ I_3 = 1 \end{array} \right.$  Unique solution case

(b) The voltage drop across a resistor is given by  
 Ohm's Law:  $V_R = RI$

$$\text{Drop across } R_1 = 4 \text{ }\Omega: V_{R_1} = R_1 I_1 = 20$$

$$\text{Drop across } R_2 = 2 \text{ }\Omega: V_{R_2} = R_2 I_2 = 8$$

$$\text{Drop across } R_3 = 1 \text{ }\Omega: V_{R_3} = R_3 I_3 = 1$$